



RTL INNOVATE HACKFEST

Design a smart 3
floor elevator controller.

TEAM NAME: VTX (Verilog vortex)

Members:

1. Ananya Chaturvedi
(202501101200008)
2. Srishti Prajapati

(202501101200032)


Problem statement :

Design an elevator controller for 3 floor which handles the request, controls the direction and the door timings using FSM(finite State Machine).


Approach:

Using Moore FSM, we have tried to implement a smart elevator controller for 3 floor,

Block diagram:

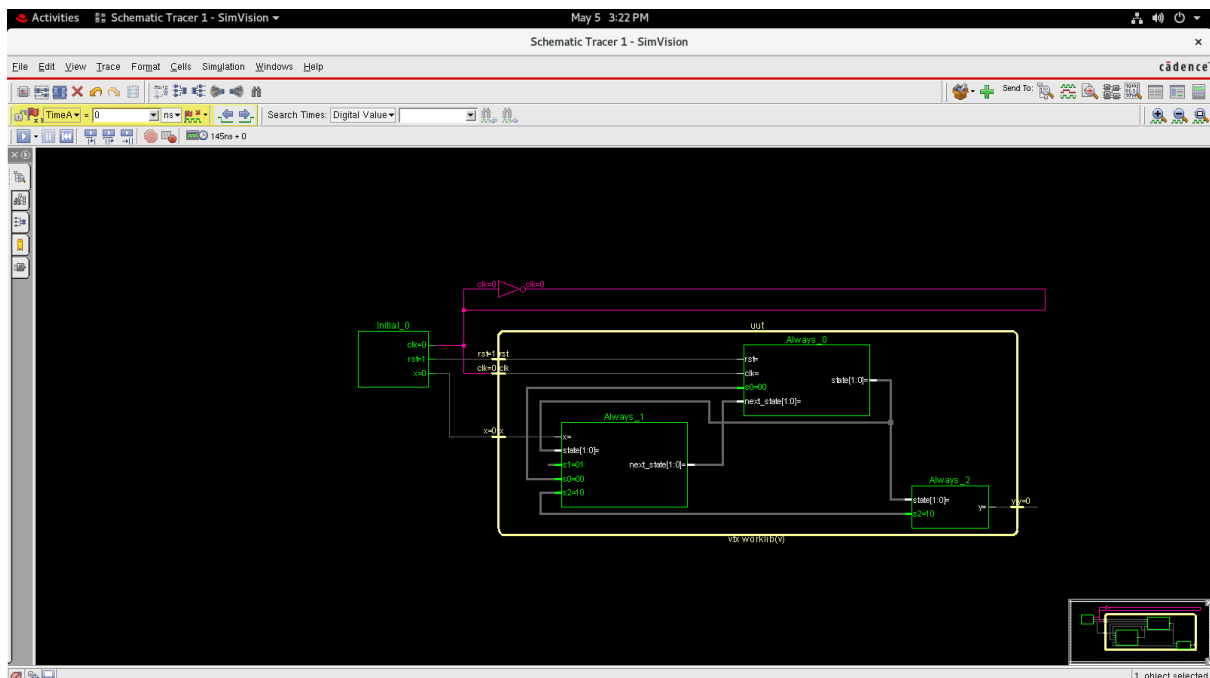

Code explanation:

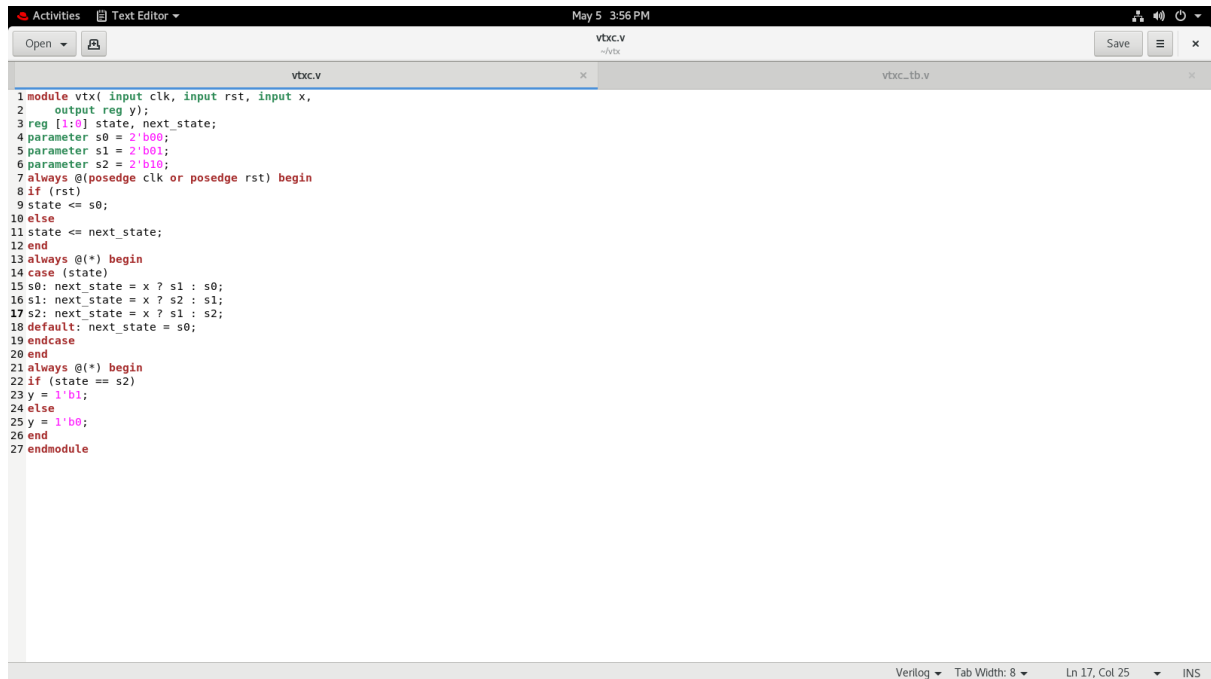


```
1 module vtx( input clk, input rst, input x,
2   output reg y);
3   reg [1:0] state, next_state;
4   parameter s0 = 2'b00;
5   parameter s1 = 2'b01;
6   parameter s2 = 2'b10;
7   always @(posedge clk or posedge rst) begin
8     if (rst)
9       state <= s0;
10    else
11      state <= next_state;
12    end
13    always @(*) begin
14      case (state)
15        s0: next_state = x ? s1 : s0;
16        s1: next_state = x ? s2 : s1;
17        s2: next_state = x ? s1 : s2;
18        default: next_state = s0;
19      endcase
20    end
21    always @(*) begin
22      if (state == s2)
23        y = 1'b1;
24      else
25        y = 1'b0;
26      end
27    endmodule
```

We took 3 parameters for 3 floors(floor 0, floor1, and floor 2).

When reset(rst) is high, it denotes IDLE state in our case, which means we have no pending requests.

Next, for each state, when the input is high, it works as a up counter i.e. the elevator moves to the next floor else remains on the same floor. BUT in the case of 2nd floor, when the input is high, it acts as a down counter i.e. the elevator moves to the first floor otherwise remains on the same.

Testbench details:

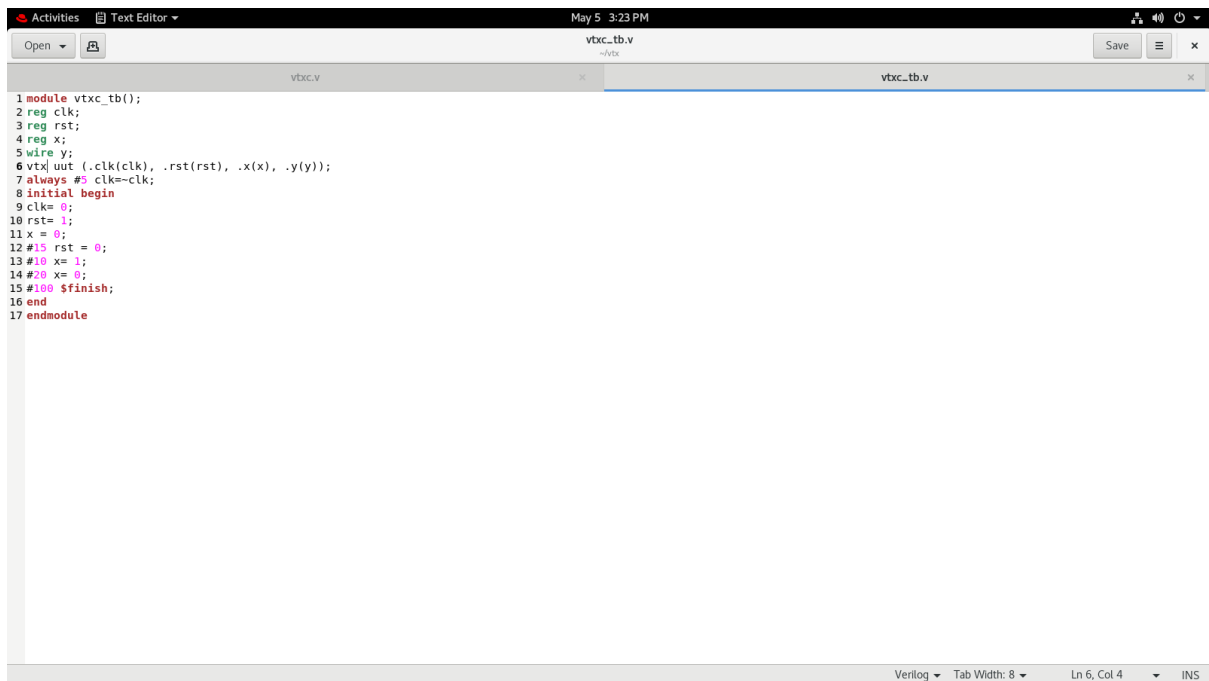

```
1 module vtxc_tb();
2 reg clk;
3 reg rst;
4 reg x;
5 wire y;
6 vtx uut (.clk(clk), .rst(rst), .x(x), .y(y));
7 always #5 clk=-clk;
8 initial begin
9   clk= 0;
10  rst= 1;
11  x = 0;
12  #15 rst = 0;
13  #10 x= 1;
14  #20 x= 0;
15  #100 $finish;
16 end
17 endmodule
```

Waveform analysis:



Challenges faced:

Code debugging.

Understanding the use of blocking and non-blocking statements.

GitHub Link:

<https://github.com/capybara-hue/ELEVATOR-DESIGN/tree/main>